

{ {<P=41><C=06><S=extension><T=SQ><M=5><L=1><X=F><id=001> } }


4162001

F E The r.m.s. value of the mains supply in Taiwan is 110 V.

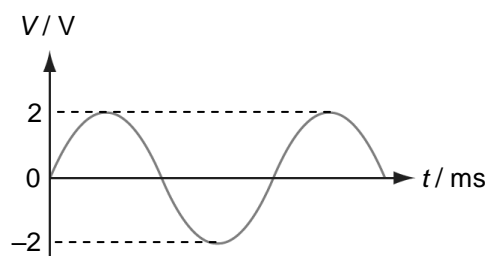- (a) Calculate the peak voltage of the mains. (2 marks)
- (b) A resistor of $100\ \Omega$ is connected to the mains supply.
 - (i) Find the average power developed in the resistor. (2 marks)
 - (ii) A steady voltage V_{dc} is now applied to the resistor. What should be the value of V_{dc} to maintain the same average power as in (i)? (1 mark)

4162002


F E A student connects an a.c. source to a $10\text{-}\Omega$ resistor and a CRO. The figure below shows the trace on the CRO.



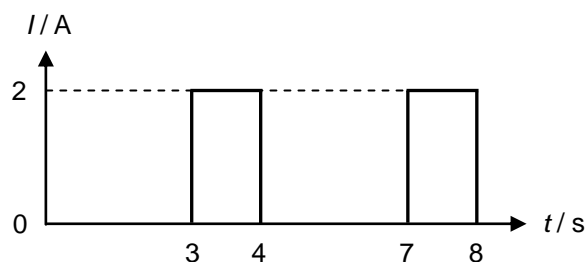- (a) What is the peak-to-peak value of the voltage? (1 mark)
- (b) Find the maximum power of the resistor. (2 marks)
- (c) Find the r.m.s. value of voltage. (2 marks)
- (d) Hence, find the average power of the resistor. (2 marks)

4162003


F E The figure below shows the variation of a current I with time t .



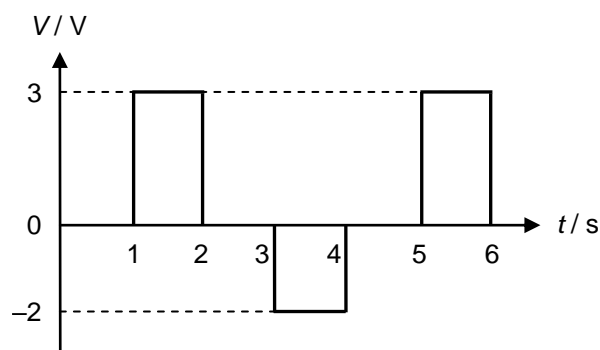- (a) Is the current shown above an a.c. or a d.c.? (1 mark)
- (b) Find the mean value of the current. (2 marks)
- (c) Find the root-mean-square value of the current. (2 marks)
- (d) The current above is then allowed to pass through a resistor. If another steady current I_1 gives the same heating effect in the same resistor in the same time as this current does, what is I_1 ? (1 mark)

4162004


FE The voltage V of an a.c. source varies with time t as shown.



- Find the mean value of the voltage. (2 marks)
- Find the root-mean-square value of the voltage. (2 marks)
- If the voltage is applied to a $15\text{-}\Omega$ resistor, what is the average power dissipated by the resistor? (2 marks)

4162005

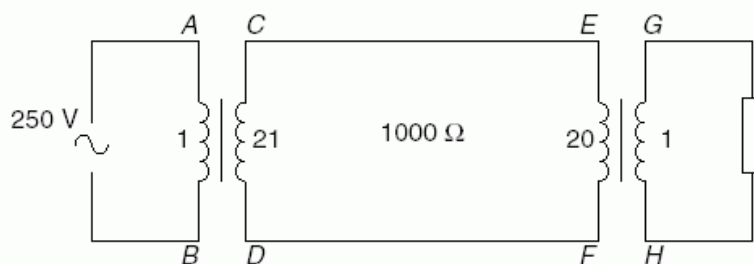
E The following figure shows a power line for transmitting electrical power from a power station to a factory. The station generates electricity at 250 V a.c. A step-up transformer of turns ratio 1 : 21 is used at the power station side of the power line and a step-down transformer of turns ratio 20 : 1 is used at the factory side.



- Calculate the voltage across CD . (2 marks)
- The power line has a resistance of $1000\ \Omega$ and the current through the line is 0.25 A .
 - Calculate the voltage drop along the power line. (2 marks)
 - What is the voltage across GH ? (2 marks)

4162006

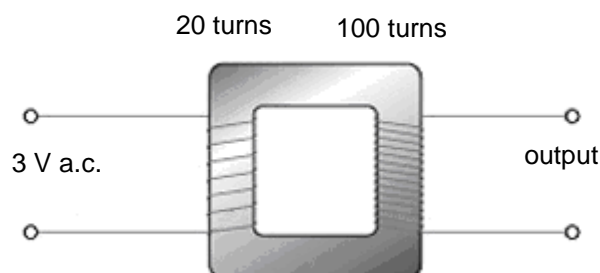E The following transformer is connected to a 3-V a.c. supply.



- (a) If the current in the secondary coil is 0.1 A and the power loss in the transformer is 0.3 W, what is the primary current? (4 marks)
- (b) Suggest two methods to increase the efficiency of the transformer. (2 marks)

4162007

★


E The input voltage and current of a transformer for a computer hub are 240 V and 120 mA respectively.

- (a) Find the input power of the transformer. (2 marks)
- (b) If the efficiency of the transformer is 87%, find the power loss in the transformer. (2 marks)
- (c) Suggest a main reason for the power loss. In what form of energy is lost in the transformer? (2 marks)

4162008

★

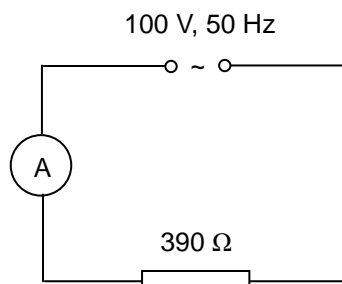F E In the figure below, an ammeter of internal resistance $10\ \Omega$ and a $390\text{-}\Omega$ resistor are connected to an a.c. power supply. The root-mean-square value of the voltage and the frequency of the power supply are 100 V and 50 Hz respectively.



- (a) What is the r.m.s. value of the current in this circuit? (3 marks)

- (b) What is the r.m.s. value of the voltage across the $390\text{-}\Omega$ resistor? (2 marks)
- (c) What is the peak value of the current in the circuit? (2 marks)
- (d) What is the maximum power dissipated by the $390\text{-}\Omega$ resistor? (2 marks)

4162009


★

- F E**
- (a) What is meant by ‘the effective value of an a.c.’? (2 marks)
 - (b) What is the relationship between the effective value I_e and the r.m.s. value I_{rms} of an a.c.? (1 mark)
 - (c) What is the relationship between the peak value I_0 and the r.m.s. value I_{rms} of a sinusoidal alternating current? (1 mark)
 - (d) If the value of a steady direct current and the peak value of a sinusoidal alternating current are equal, calculate the ratio of the average power dissipated by a resistor of resistance R by the direct current to that by the alternating current. (2 marks)

4162010

★

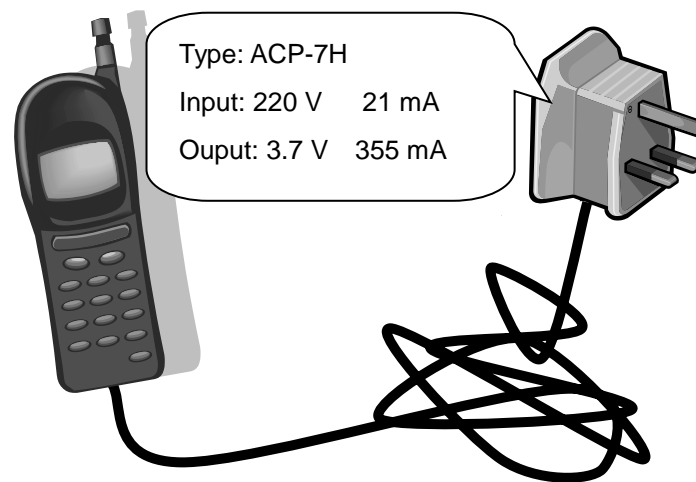- E** The label on a mobile phone charger is shown below.




There is a transformer in the charger.

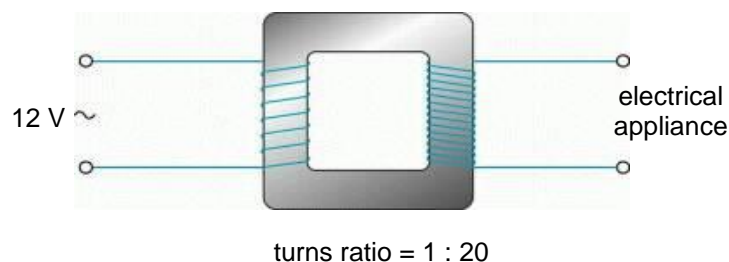- (a) Is it a step-up transformer or a step-down transformer? (1 mark)
- (b) Find the turns ratio of the transformer. (2 marks)
- (c) Calculate the efficiency of the transformer. (3 marks)

4162011



- E** The following figure shows a transformer with turns ratio 1 : 20. The primary coil is connected to a 12 V a.c. power supply to operate an electrical appliance connected to the secondary coil.




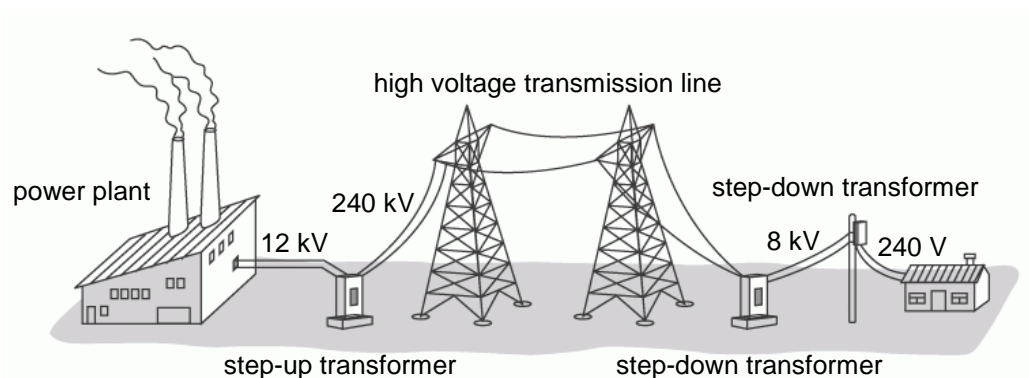- (a) What is the type of the transformer, step-up or step-down? Explain your answer briefly. (2 marks)
- (b) Suppose that the primary current of the transformer is 125 A and the current through the electrical appliance is 5 A. Find the efficiency of the transformer. (4 marks)
- (c) State two methods to increase the efficiency of a transformer. (2 marks)

4162012



- E** The following figure shows how electricity is transmitted from a power plant to households.



- (a) (i) The step-up transformer changes the voltage from 12 000 V to a higher value of 240 000 V. What is the turns ratio of the transformer? (2 marks)
- (ii) Does the step-up transformer also change the transferred energy to a higher value? (1 mark)

- (b) The power output of the power plant is 36 MW. The total resistance of the transmission line is known to be $150\ \Omega$.
- Find the current through the transmission line by assuming the step-up transformer is ideal. (3 marks)
 - Hence, find the percentage loss of power in the transmission line. (3 marks)

4162013


★★

- F E** (a) What is meant by the ‘peak value’ and the ‘effective value’ of an alternating current? (3 marks)
- (b) A sinusoidal alternating current can be expressed as $I = 24 \sin 100\pi t$. Find
- the frequency
 - the peak value
 - the effective value
- of this alternating current. (4 marks)

4162014

★★

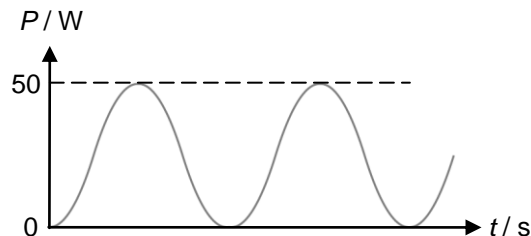- F E** The graph below shows how the input power of a transformer varies with time.



The turns ratio of the transformer is 1 : 150 and the r.m.s. value of the primary voltage is 6 V. Assuming that the transformer is ideal, calculate

- the r.m.s. value of the secondary voltage, (2 marks)
- the average input power, (2 marks)
- the r.m.s. value of the primary current, and (2 marks)
- the r.m.s. value of the secondary current. (2 marks)